


ECEN 454 - Lab 4 Report  
Luke Lopez

# Report


Some changes have been made to the fundamental circuit designs, to see these changes and the new models, see **Appendix A** at the bottom of this report.

## 1 Bit adder

### Schematic

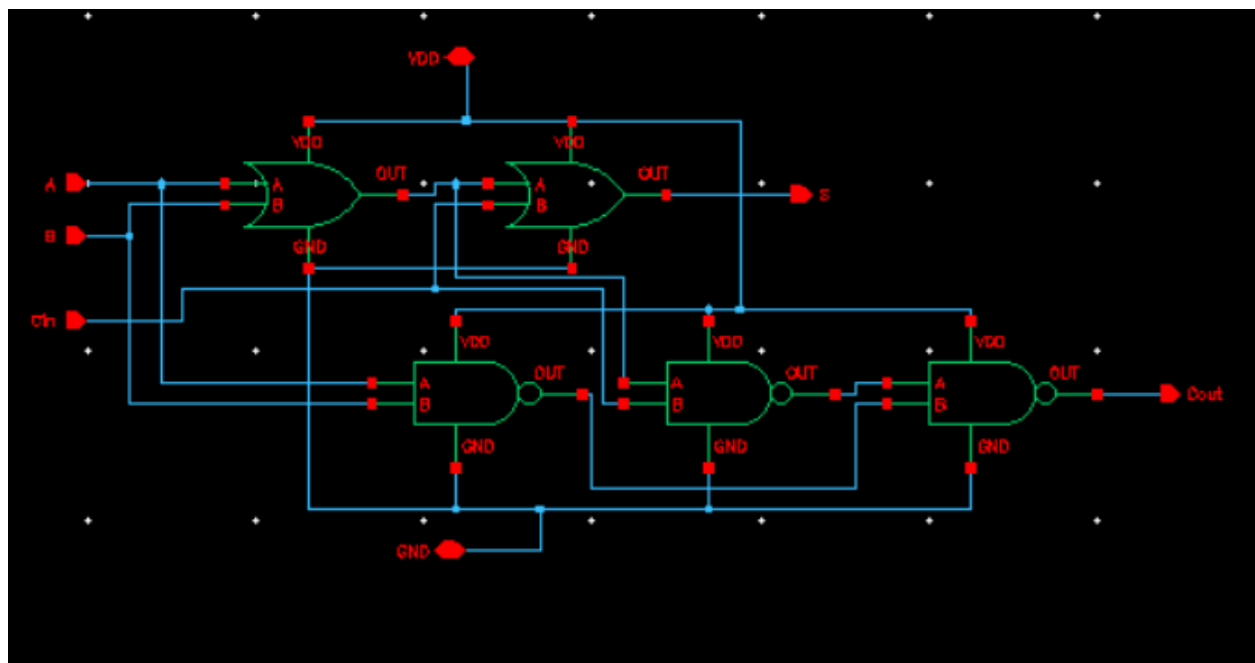

## Layout

 

## DRC

```
DRC started.....Wed Oct 22 22:21:31 2025
completed ....Wed Oct 22 22:21:31 2025
CPU TIME = 00:00:00  TOTAL TIME = 00:00:00
***** Summary of rule violations for cell "1bAdder layout" *****
Total errors found: 0
```

# LVS

Compiling Diva LVS rules...

Net-list summary for /home/ugrads/s/skywalker499/454-ECEN/LVS/layout/netlist

count	
40	nets
7	terminals
360	pmos
164	nmos

Net-list summary for /home/ugrads/s/skywalker499/454-ECEN/LVS/schematic/netlist

count	
25	nets
7	terminals
18	pmos
18	nmos

Terminal correspondence points

N36	N2	A
N35	N5	B
N37	N6	Cin
N38	N4	Cout
N33	N1	GND
N34	N3	S
N39	N0	VDD

Devices in the rules but not in the netlist:

cap nfet pfet nmos4 pmos4

The net-lists match.


## Rising and Falling Delays


Device	Rising Delay	Falling Delay	Error
Inverter	60.65 ps	55.15 ps	9.97%
NAND2	425.1 ps	486.3 ps	7.56%
XOR2	152 ps	147 ps	3.4%


1bAdder	Rising	Fall
S	178 ps	165.8 ps
Cout	139.4 ps	129.7 ps

# Waveform of outputs

## Inverter

 


 

 




# NAND2

 

# XOR2

 


## 1 Bit adder

# Power Dissipations

Device	Power of Vdd	Power A	Power B	Power Cin
Inverter	5.103 $\mu$ W	0.813 $\mu$ W	N/A	N/A
NAND2	68.61 $\mu$ W	0.565 nW	34.03 nW	N/A
XOR2	25.34 $\mu$ W	0.01122 $\mu$ W	0.01202 $\mu$ W	N/A
1 Bit Adder	80.5 $\mu$ W	0.25 $\mu$ W	0.33 $\mu$ W	0.576 $\mu$ W

 Maximum Frequency :  $1/2\text{ns} = 500 \text{ MHz}$



Note: there are some anomalies when two signals are changing not at the same time, but their values overlap. However it can be seen that when the signals change at the same time (like when a clock is implemented) the system works fine.

## APPENDIX A: Changes to previous systems

### Notes on changes:


All lengths are the same at **0.2u m**

Additionally, to increase the speed, and maximum frequency, I reduced the capacitance of the transistors by having an intertwined layout design, where some transistors share drains or sources. This reduces the total capacitance area of the transistors. This is easily seen in the layout pictures.


Device	Pmos	Nmos
XOR	10u	3u
Inverter	10u	3u
NAND	10u	5u

# Inverter

## Schematic

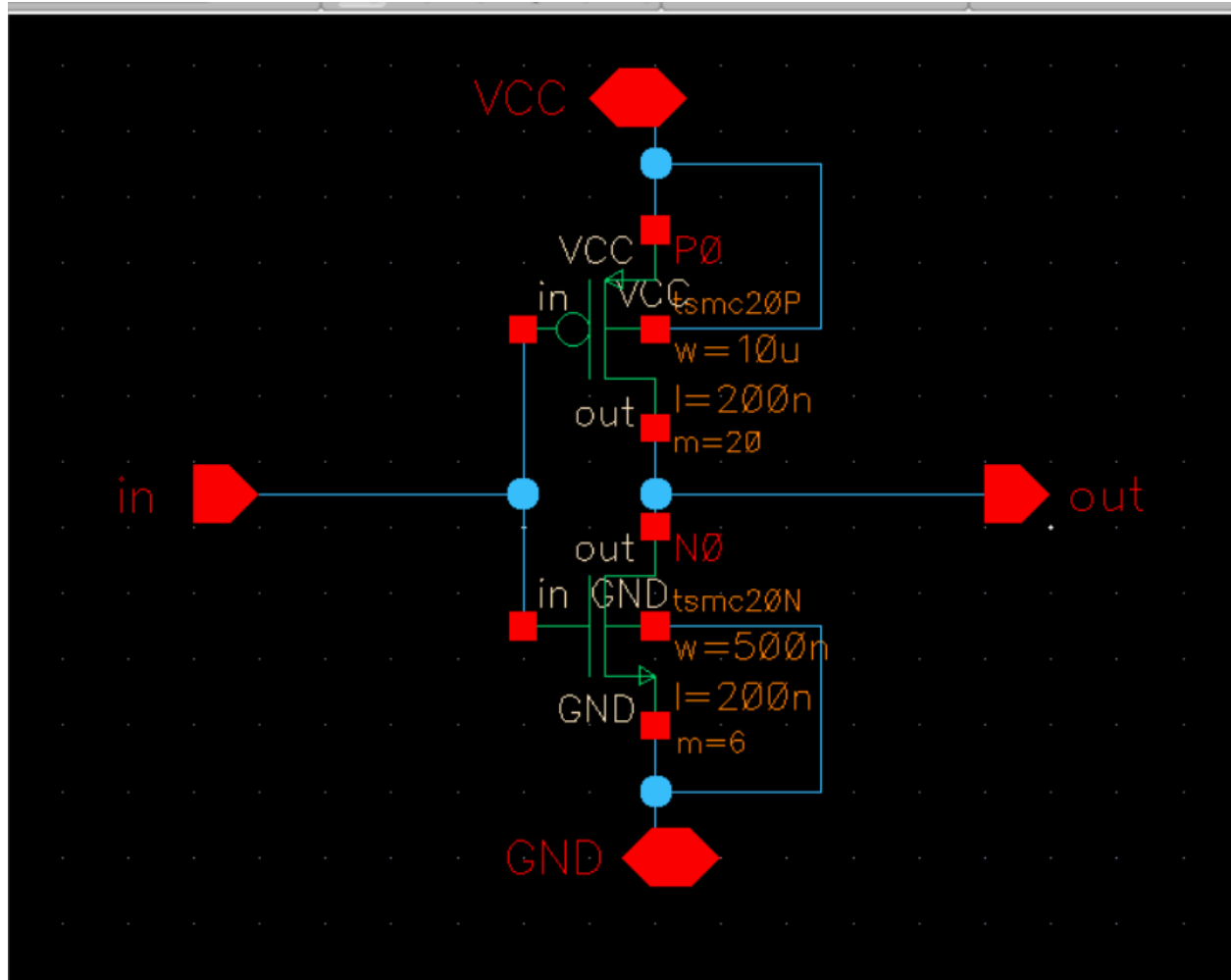

# Layout

 

## DRC

```
Running layout DRC analysis
Flat mode
Full checking.
DRC started.....Wed Oct 22 15:31:34 2025
completed ....Wed Oct 22 15:31:34 2025
CPU TIME = 00:00:00 TOTAL TIME = 00:00:00
***** Summary of rule violations for cell "inverter layout" *****
Total errors found: 0
```

# LVS

Compiling Diva LVS rules...

Net-list summary for /home/ugrads/s/skywalker499/454-ECEN/LVS/layout/netlist

count	
4	nets
4	terminals
20	pmos
6	nmos

Net-list summary for /home/ugrads/s/skywalker499/454-ECEN/LVS/schematic/netlist

count	
4	nets
4	terminals
1	pmos
1	nmos

Terminal correspondence points

N1	N1	GND
N0	N0	VCC
N3	N3	in
N2	N2	out


Devices in the rules but not in the netlist:

cap nfet pfet nmos4 pmos4

The net-lists match.


## NAND2

## Schematic

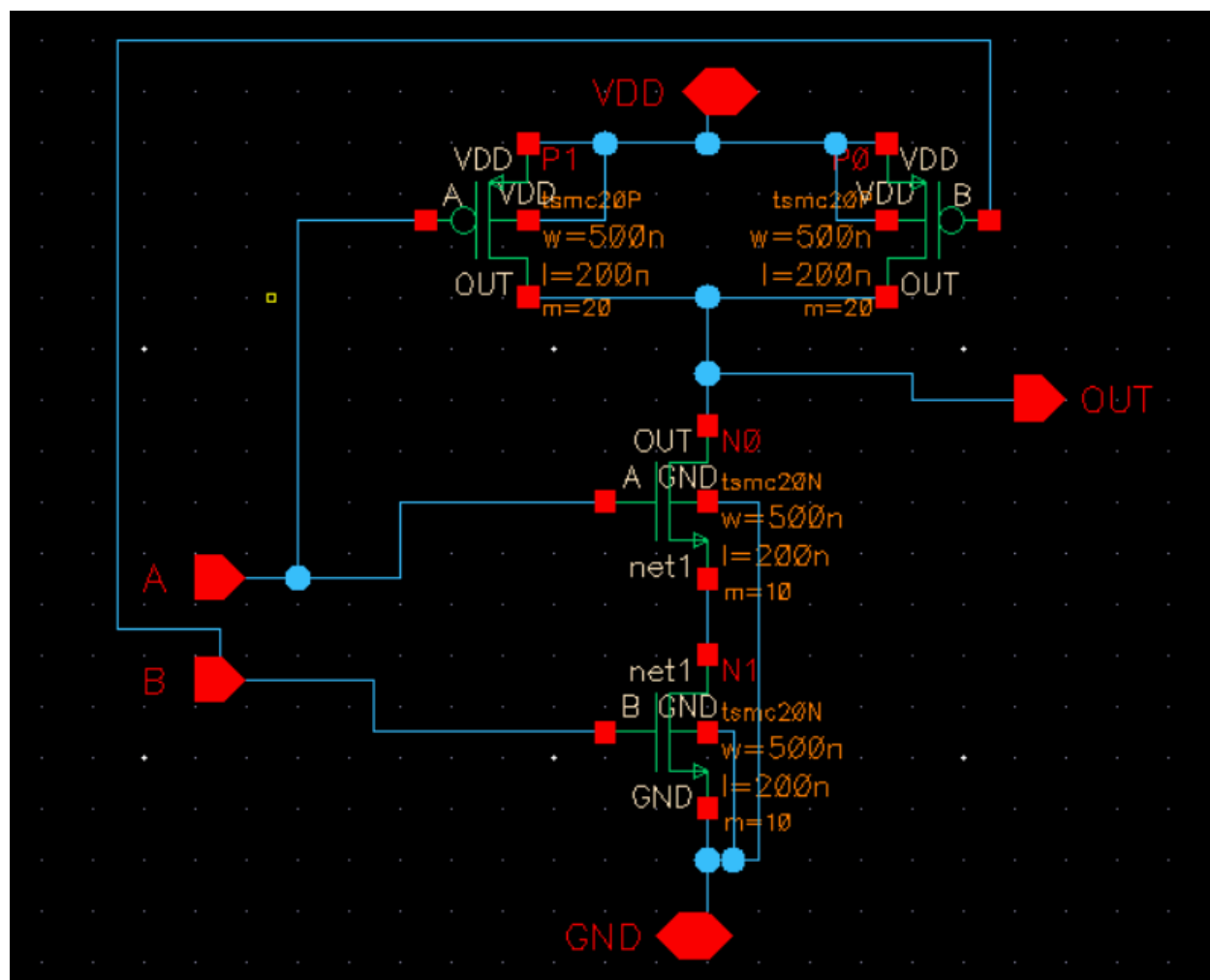



## Layout

 

## DRC

```
Running layout DRC analysis
Flat mode
Full checking.
DRC started.....Wed Oct 22 15:39:43 2025
  completed ....Wed Oct 22 15:39:43 2025
  CPU TIME = 00:00:00  TOTAL TIME = 00:00:00
***** Summary of rule violations for cell "NAND2 layout" *****
Total errors found: 0
```

# LVS

Compiling Diva LVS rules...

Net-list summary for /home/ugrads/s/skywalker499/454-ECEN/LVS/layout/netlist

count	
4	nets
4	terminals
20	pmos
6	nmos

Net-list summary for /home/ugrads/s/skywalker499/454-ECEN/LVS/schematic/netlist

count	
4	nets
4	terminals
1	pmos
1	nmos

Terminal correspondence points

N1	N1	GND
N0	N0	VCC
N3	N3	in
N2	N2	out


Devices in the rules but not in the netlist:

cap nfet pfet nmos4 pmos4


The net-lists match.

# XOR2

## Schematic

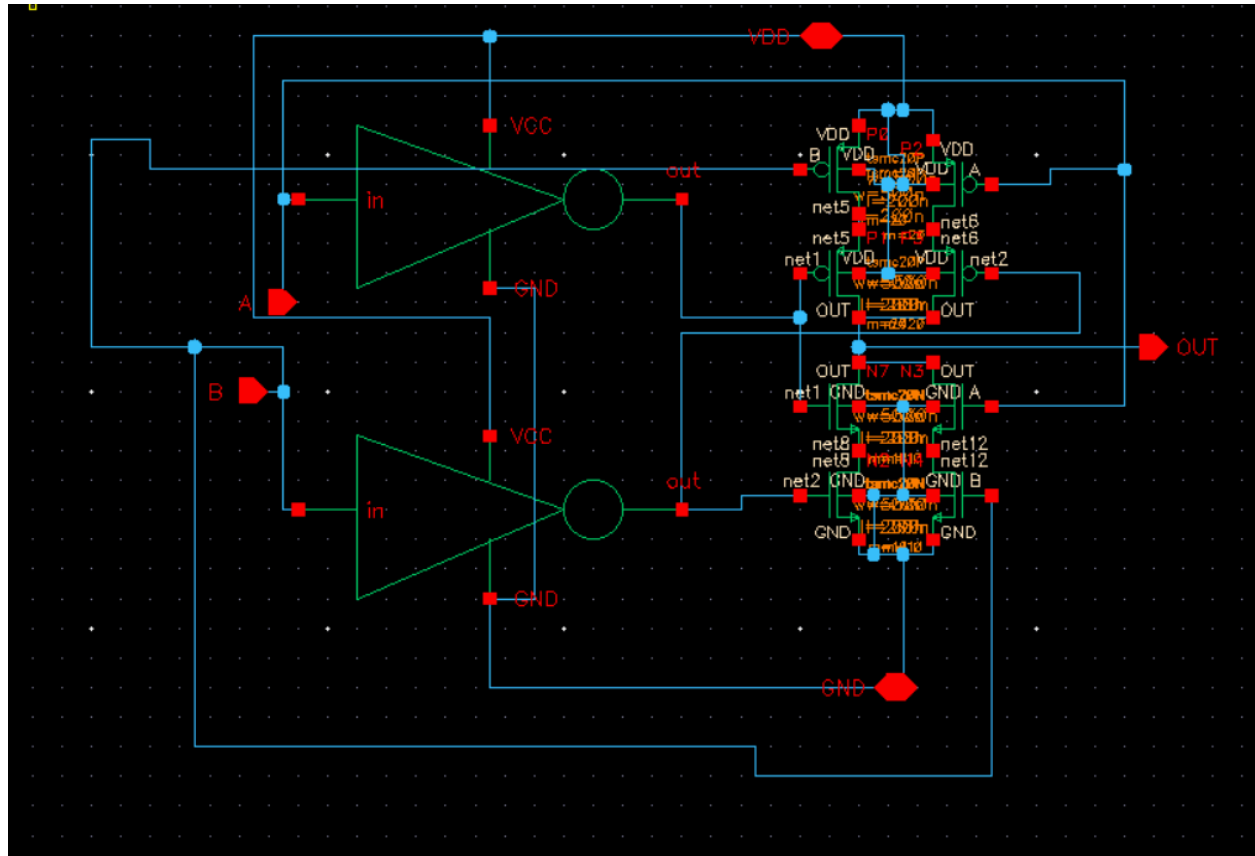

# Layout

 

## DRC

```
Running layout DRC analysis
Flat mode
Full checking.
DRC started.....Wed Oct 22 15:45:09 2025
  completed ....Wed Oct 22 15:45:09 2025
  CPU TIME = 00:00:00  TOTAL TIME = 00:00:00
***** Summary of rule violations for cell "XOR2 layout" *****
Total errors found: 0
```

## LVS

```
Compiling Diva LVS rules...

Net-list summary for /home/ugrads/s/skywalker499/454-ECEN/LVS/layout/netlist
count
  4      nets
  4      terminals
 20      pmos
  6      nmos

Net-list summary for /home/ugrads/s/skywalker499/454-ECEN/LVS/schematic/netlist
count
  4      nets
  4      terminals
  1      pmos
  1      nmos

Terminal correspondence points
N1      N1      GND
N0      N0      VCC
N3      N3      in
N2      N2      out

Devices in the rules but not in the netlist:
  cap nfet pfet nmos4 pmos4

The net-lists match.
```

## APPENDIX B: General Calculator input used

```
Delay_F
value(delay(?wf1 v("/out" ?result "tran") ?value1 0.9 ?edge1 "rising" ?nth1 1 ?td1 0.0 ?tol1 nil
?wf2 v("/A" ?result "tran") ?value2 0.9 ?edge2 "falling" ?nth2 1 ?tol2 nil ?td2 nil ?stop nil
?period1 1 ?period2 1 ?multiple t ?xName "trigger") 0)
```

Delay\_R

```
value(delay(?wf1 v("/out" ?result "tran") ?value1 0.9 ?edge1 "falling" ?nth1 1 ?td1 0.0 ?tol1 nil
?wf2 v("/B" ?result "tran") ?value2 0.9 ?edge2 "rising" ?nth2 1 ?tol2 nil ?td2 nil ?stop nil
?period1 1 ?period2 1 ?multiple t ?xName "trigger") 0)
```

```
Power_vdd
(average(i("/V2/PLUS" ?result "tran")) * 1.8)
```

```
Power_A
(average(i("/I1/A" ?result "tran")) * average(v("/A" ?result "tran")))
```

```
Power_B
(average(i("/I1/B" ?result "tran")) * average(v("/B" ?result "tran")))
```