


ECEN 454 - Lab 1 Report

Luke Lopez


09/08/2025

# Schematics


## Full Adder

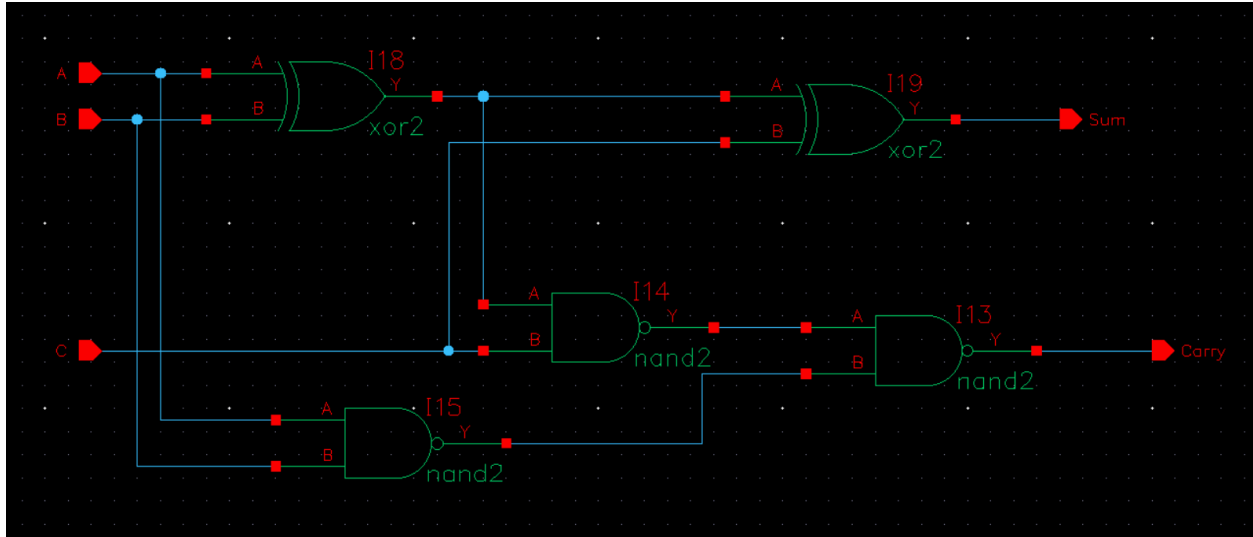


## 4-Bit-Adder

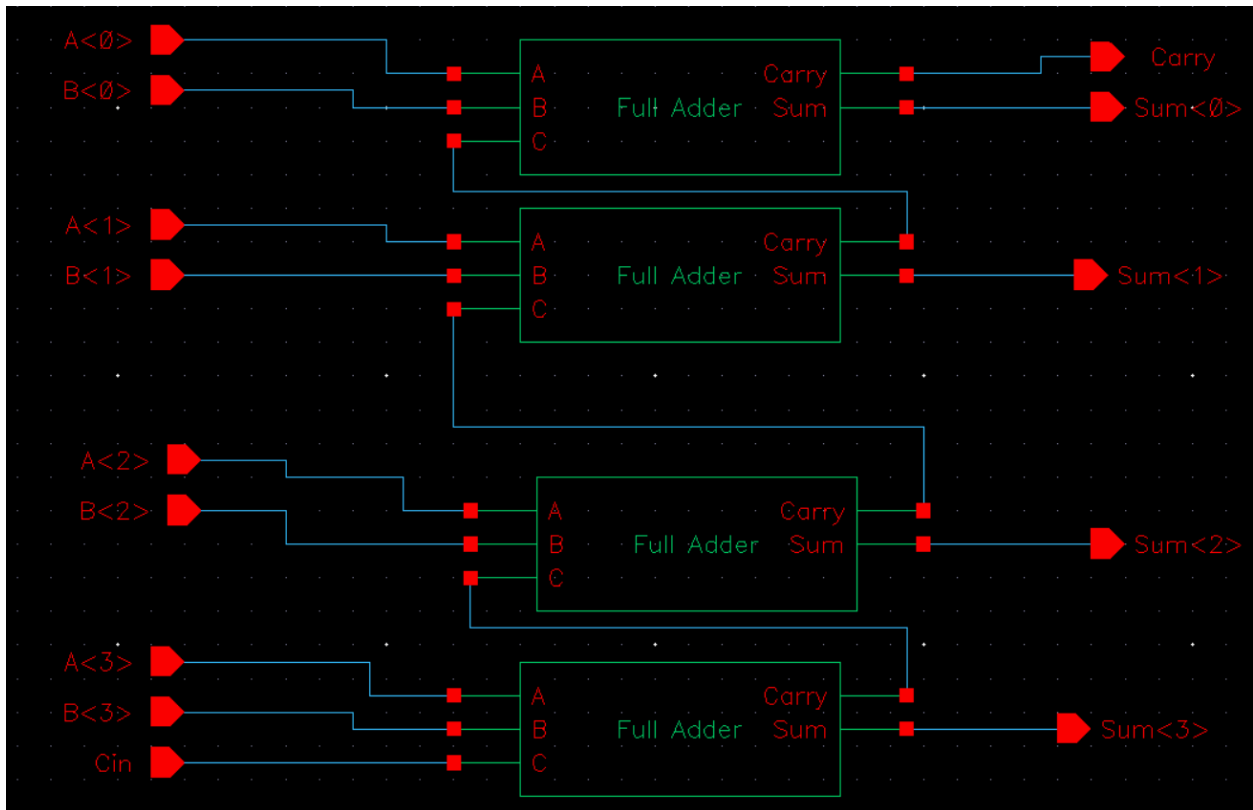


## 8-Bit-Adder

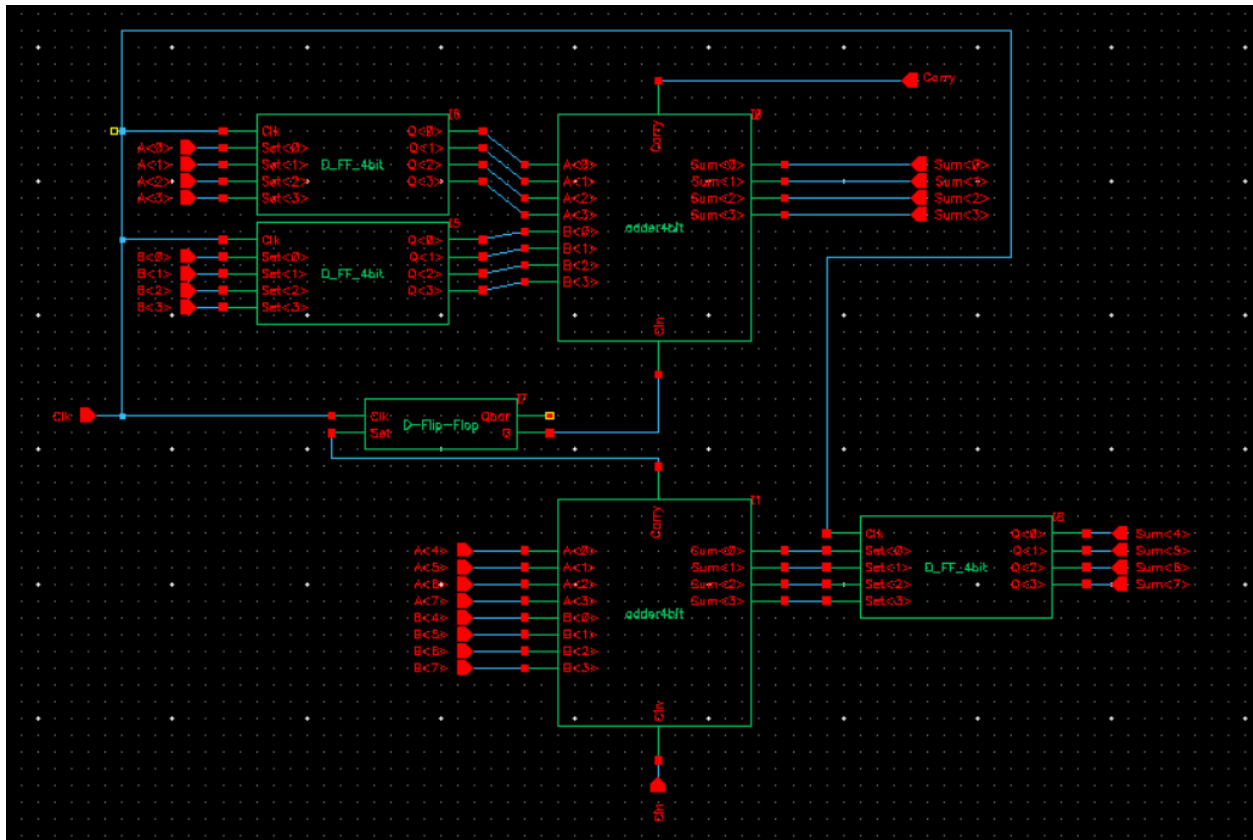

## D-Flip Flop

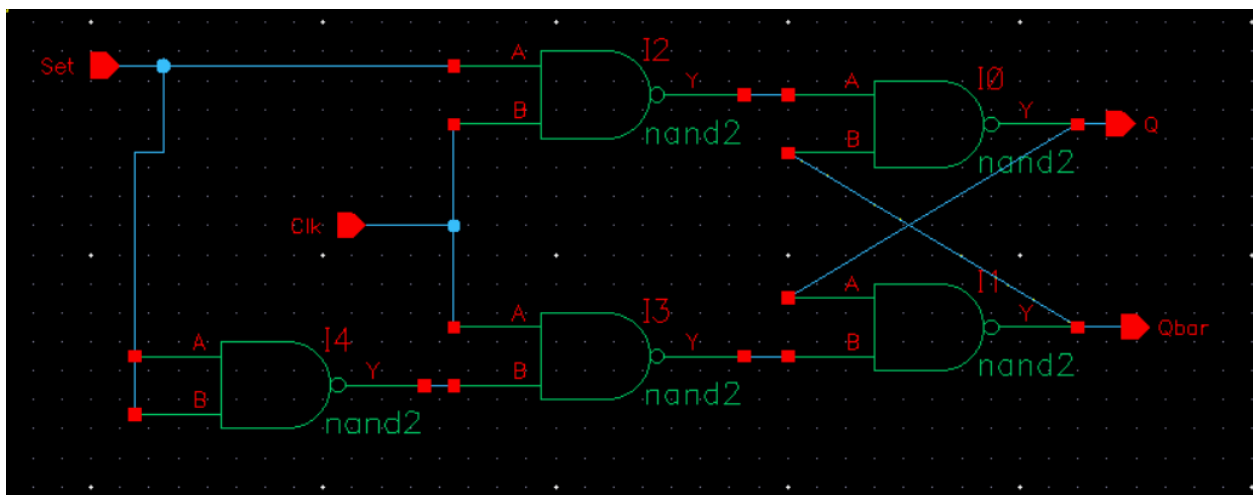

## 4Bit-Flip-Flop

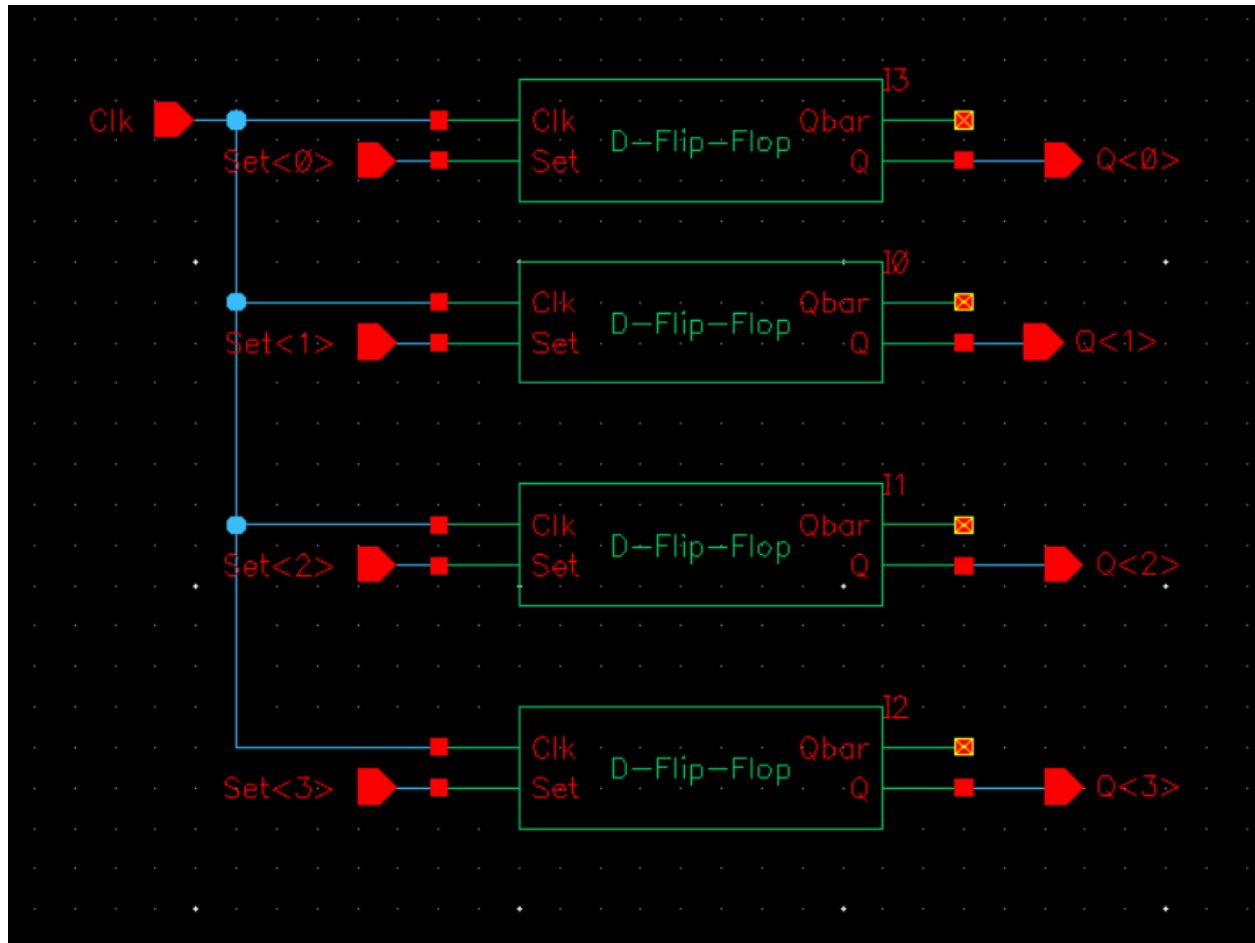


# Symbols


## Full Adder



## 4-Bit Adder

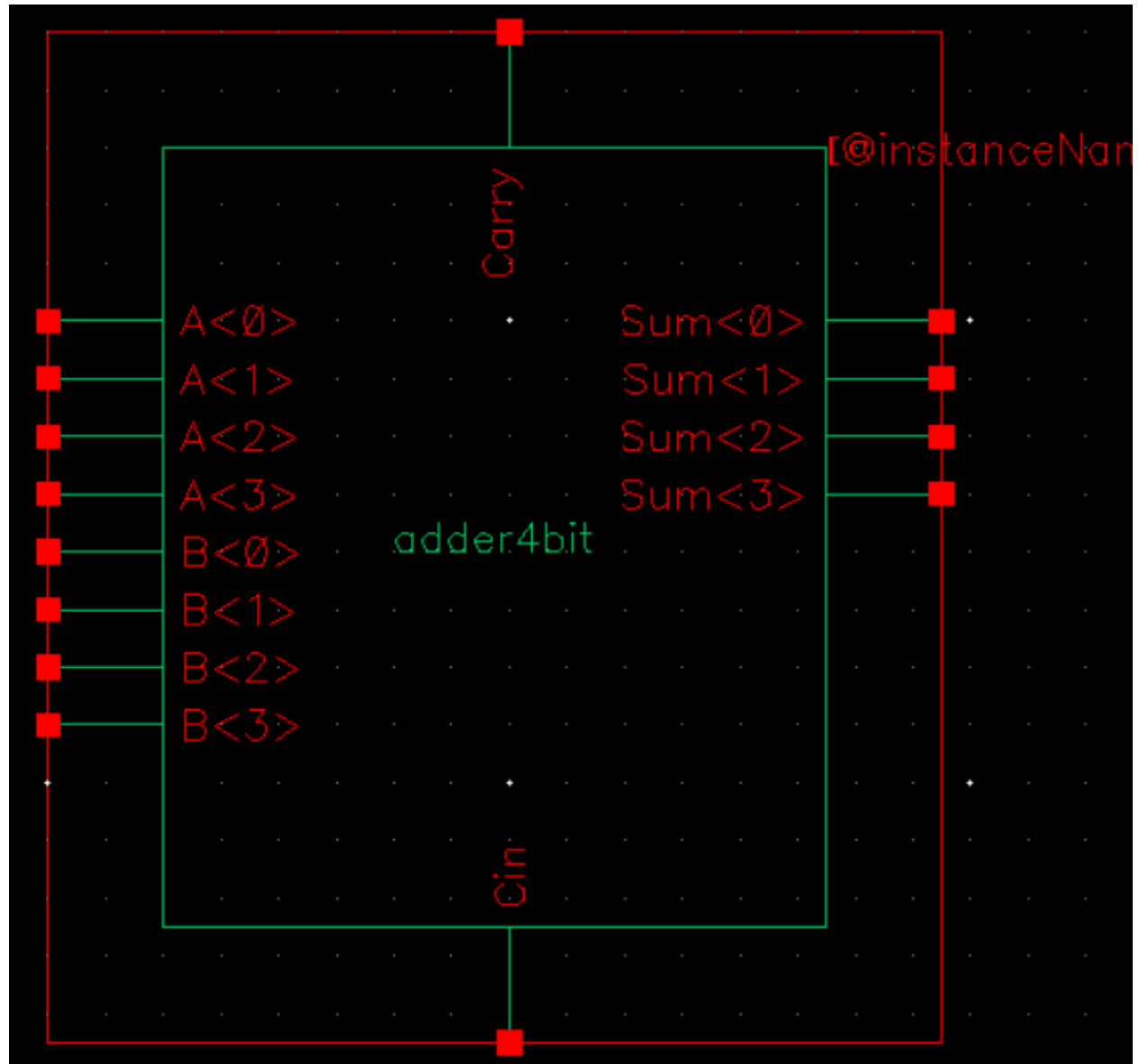


## 8-Bit-Adder

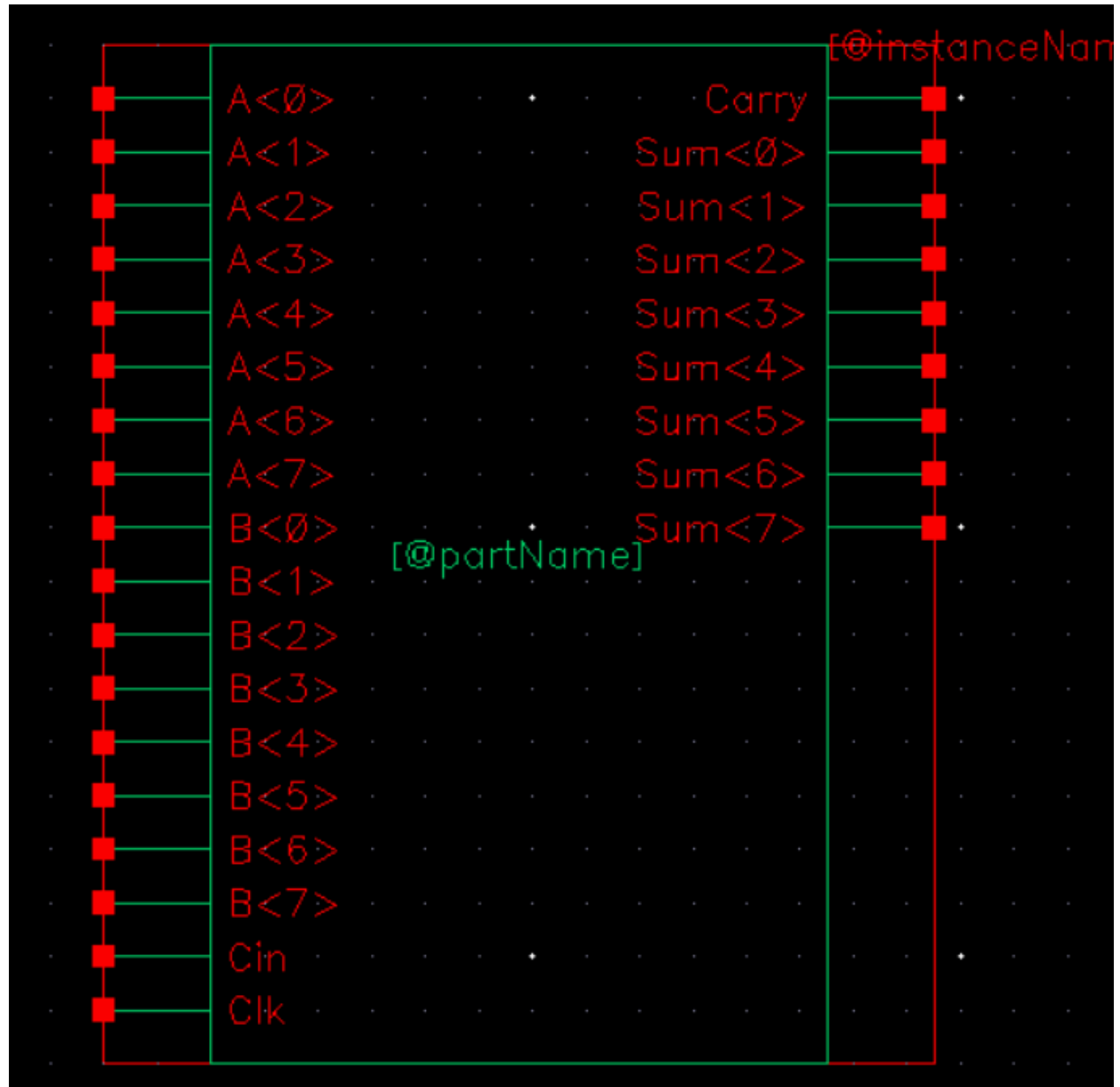

# Simulation Results

NOTE: In most simulations, there is a “Fail” variable that shows the number of fails done while testing. In all graphics it can be seen that no fails occurred.

## Full-Adder

 

Test type: Directed Full Adder (A, B, C inputs)

Full adder:  $0 + 0 + 0$  (Cin) = Sum=0 Carry=0  
Full adder:  $0 + 0 + 1$  (Cin) = Sum=1 Carry=0  
Full adder:  $0 + 1 + 0$  (Cin) = Sum=1 Carry=0  
Full adder:  $0 + 1 + 1$  (Cin) = Sum=0 Carry=1  
Full adder:  $1 + 0 + 0$  (Cin) = Sum=1 Carry=0  
Full adder:  $1 + 0 + 1$  (Cin) = Sum=0 Carry=1  
Full adder:  $1 + 1 + 0$  (Cin) = Sum=0 Carry=1  
Full adder:  $1 + 1 + 1$  (Cin) = Sum=1 Carry=1


All tests complete. Total fails: 0

## Notes

The test results all come out correct. Whenever there is more than 1 inputs with VAL 1, Carry = 1. Additionally, the Sums are all calculated correctly.



## 4-Bit-Adder

 


4bit adder: 0000 + 0000 + 0 (Carry In) = 0000 (Carry Out = 0)  
4bit adder: 0000 + 0000 + 1 (Carry In) = 0001 (Carry Out = 0)  
4bit adder: 0000 + 0001 + 0 (Carry In) = 0001 (Carry Out = 0)  
4bit adder: 0000 + 0001 + 1 (Carry In) = 0010 (Carry Out = 0)  
4bit adder: 1111 + 1111 + 0 (Carry In) = 1110 (Carry Out = 1)  
4bit adder: 1111 + 1111 + 1 (Carry In) = 1111 (Carry Out = 1)  
4bit adder: 1110 + 0100 + 1 (Carry In) = 0011 (Carry Out = 1)  
4bit adder: 1110 + 0101 + 0 (Carry In) = 0011 (Carry Out = 1)  
4bit adder: 0101 + 0101 + 1 (Carry In) = 1011 (Carry Out = 0)  
4bit adder: 0101 + 0110 + 0 (Carry In) = 1011 (Carry Out = 0)

## Notes

I did an exhaustive test on the 4 bit adder and had the verilog code check the outputs and all of them passed. However I did print out some edge cases and random ones too, and as you can see, the addition checks out.

## 8-Bit adder

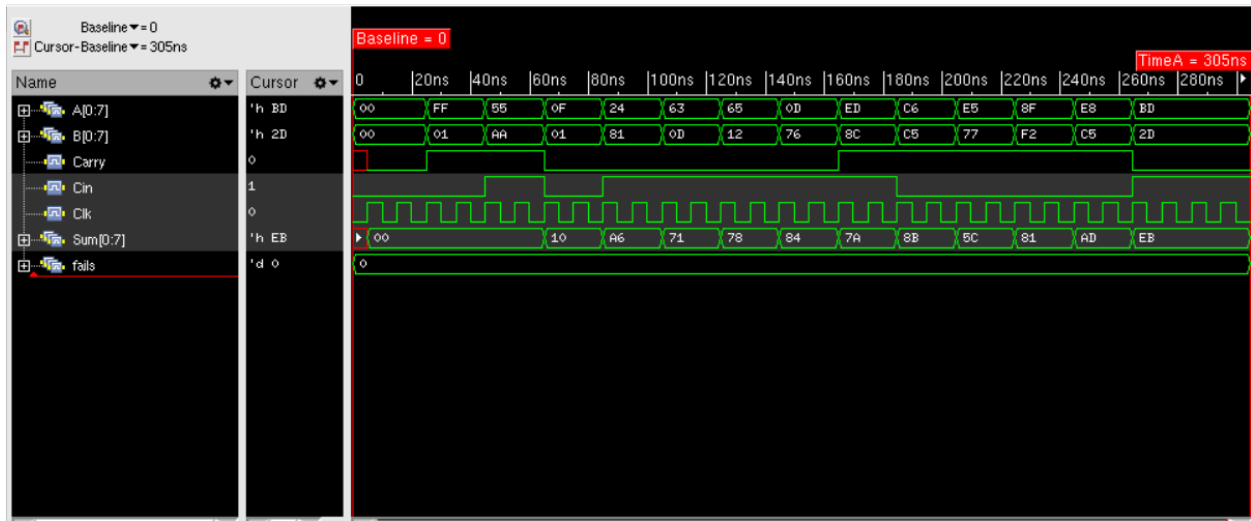

Starting 8-bit adder test with pipeline delay...

8bit adder: 01111110 + 11100111 + 0 (Carry In) = 01100101 (Carry Out = 1)  
8bit adder: 11111111 + 00000000 + 1 (Carry In) = 00000000 (Carry Out = 1)  
8bit adder: 10101010 + 01010101 + 0 (Carry In) = 11111111 (Carry Out = 0)  
8bit adder: 10101010 + 01010101 + 1 (Carry In) = 00000000 (Carry Out = 1)  
8bit adder: 11001100 + 00110011 + 0 (Carry In) = 11111111 (Carry Out = 0)  
8bit adder: 11001100 + 00110011 + 1 (Carry In) = 00000000 (Carry Out = 1)  
8bit adder: 00100100 + 10000001 + 1 (Carry In) = 10100110 (Carry Out = 0)  
8bit adder: 01100011 + 00001101 + 1 (Carry In) = 01110001 (Carry Out = 0)  
8bit adder: 01100101 + 00010010 + 1 (Carry In) = 01111000 (Carry Out = 0)  
8bit adder: 00001101 + 01110110 + 1 (Carry In) = 10000100 (Carry Out = 0)

Test complete. Total fails: 0

Notes:

Since there are too many cases, I did not do an exhaustive test like the 4 bit adder, but did have most edge cases. Some of which you can see here. Again I had the verilog code check if there was any errors as it was testing, which as we can see, none occurred.

## D-Flip-Flop

