
 


ECEN 454 - Lab 9 Report
Luke Lopez

Delay Route

 

Schematics



Calculation of G

$$G = \prod g_i (i = 1, 2, 3, 4, \dots, 9)$$

$$G = 4 * \left(\frac{4}{3}\right)^8 = 40$$

$$H = C_{\text{load}} / C_{\text{xor}}$$

$$= 30 \text{ fF} / 2 \text{ fF}$$

$$= 15$$

$$b1 = (C_{\text{xor}} + C_{\text{nand2}}) / C_{\text{xor}}$$

$$= (2 \text{ fF} + 2 \text{ fF}) / 2 \text{ fF}$$

$$= 2$$

$$b2, b4, b6, b8 = (C_{\text{xor}} + C_{\text{nand2}}) / C_{\text{nand2}}$$

$$= (2 \text{ fF} + 2 \text{ fF}) / 2 \text{ fF}$$

$$= 2$$

$$b3, b5, b7, b9 = 1$$

$$B = b1 \times b2 \times b3 \times b4 \times b5 \times b6 \times b7 \times b8 \times b9$$

$$= 2 \times 2 \times 1 \times 2 \times 1 \times 2 \times 1 \times 2 \times 1$$

$$= 2^5$$

$$= 32$$

Calulations

| | |
|---|----|
| G | 40 |
| H | 15 |
| B | 32 |

$$GHB = 19200 = F$$

$$F^{1/9} = 2.99 \text{ which is within bounds of what we desired, so no resizing necessary.}$$

The transistors were all ideally sized using techniques learned in lecture. The base $w/l = 500\text{n}/200$. With W having a multiplier of 10 as a base. Then ideally sizing them for each stage.